

To get Rank (i) read notes perfectly

(ii) Volume-II (Homework) - After Completion of Syllabus


(iii) IES objective of EET, EEE

(iv) All gate bits of ECE, EEE & IN

(v) Exam practice - Mock & Gate Online Tests.

Electrical Energy — Interconvertibility
Transportation.

I

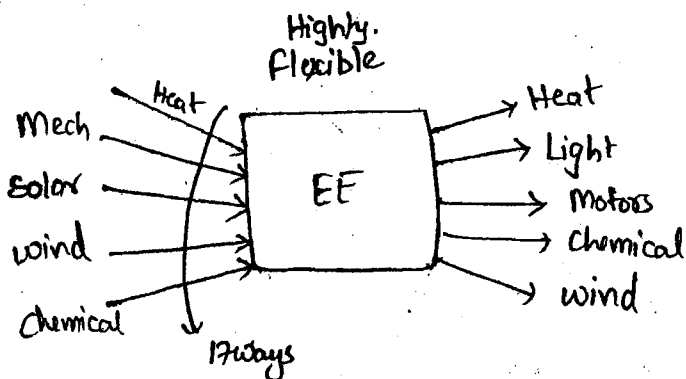

II Generation & Transportations

- * Bulk Quantities
- * Long distance
- * Most economical way.
- * cheap.

1 Unit of Electrical Energy = 1 KWH
= 1000W * 1hr .

Design Parameters:-

* Precision, Accuracy, automation, control, Portable, Compact, fast & Intelligent



Source

If Current leaves the +ve terminal
then it is called source.

Active Element




Sink

If Current leaves the -ve terminal
then it is called Sink

Passive element

Permanent Magnet:

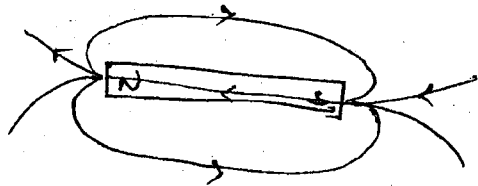$i \geq 10 \text{ mA}$ - Practical current to kill a person




Flux never moves ^{but} it is established.

R - LTI property of matter

L - Electromagnetic property of matter


C - Electrostatic property of matter


Capacitor

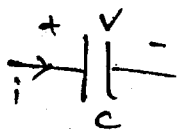

Ohm's law

$$i = C \frac{dv}{dt}$$

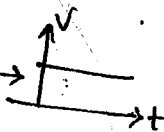DC \rightarrow  $i_c = 0$ - open ckt

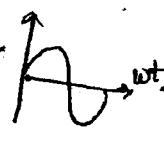AC \rightarrow  $\rightarrow I_c = I_m \sin(\omega t + 90^\circ)$

Dielectrics are special insulators which conduct with the help of polarization.


* Engineering is application of science.

Circuit

Current (i) is intended to flow through all the elements.

Condition for i to flow


- (i) EMF
- (ii) closed path.

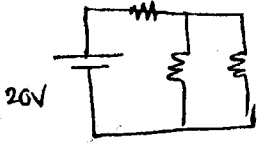

Network

No closed path & ' i ' cannot flow through all components. Circuits are building block of Networks.

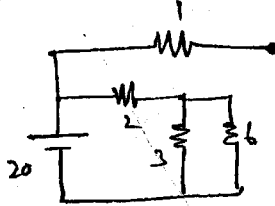- (i) EMF exists
- (ii) closed path don't exist



* Practical big interconnected systems are always networks but that path where current flows is called circuit


* Circuits are building blocks of N/w. Ex:- Communication System is a big N/w but a transmitter working in it is a circuit @ s/g level.

Our power system is a big N/w but a motor running in it is a ckt @ power level.


Network Components / Elements:-

All our practical Applications are our Components in electrical engineering. When these Components are modelled mathematically as a ckt or N/w we use fundamental N/w Components such as V, I, R, L, C etc to model the


① Heater

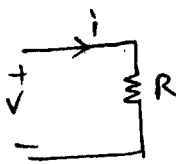

② BJT

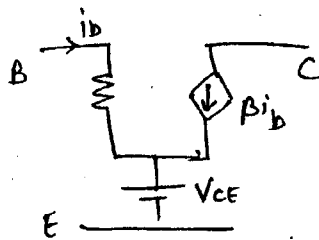

③ Fan

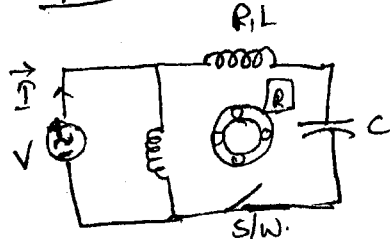

∞ impedance
 V, I, R, C, L

Ideal Voltage will have no internal R

Independent of frequency
 $V = IR$

Stores Energy, Don't create losses

Depends of frequency $V = L di/dt$

$i = C dv/dt$